
How to get the best ADC accuracy in STM32Fx Series and STM32L1 Series devices

Introduction

The STM32Fx Series and STM32L1 Series microcontroller families embed up to four advanced 12-bit ADCs (depending on the device). A self-calibration feature is provided to enhance ADC accuracy versus environmental condition changes.

In applications involving analog-to-digital conversion, ADC accuracy has an impact on the overall system quality and efficiency. To improve this accuracy, you need to understand the errors associated with the ADC and the parameters affecting them.

ADC accuracy does not depend on ADC performance and features alone, it depends on the overall application design around the ADC.

This application note aims to help understanding of ADC errors and how to enhance ADC accuracy. It is divided into three main parts:

- a simplified description of ADC internal structure to aid understanding of ADC operation and related ADC parameters
- explanations of the different types and sources of ADC errors related to the ADC design and to external ADC parameters such as the external hardware design
- recommendations on how to minimize these errors, focusing on hardware and software methods

This document applies to the products listed in [Table 1](#) which are referred to as STM32x throughout this document.

Table 1. Applicable products

Product family	Part numbers
Microcontrollers	<ul style="list-style-type: none">– STM32F0xx– STM32F1xx– STM32F2xx– STM32F3xx– STM32F4xx– STM32L1xx

Contents

- 1 **ADC internal principle** **5****
 - 1.1 SAR ADC internal structure 5

- 2 **ADC errors** **9****
 - 2.1 ADC errors related to the ADC itself 9
 - 2.1.1 Offset error 9
 - 2.1.2 Gain error 11
 - 2.1.3 Differential linearity error 12
 - 2.1.4 Integral linearity error 13
 - 2.1.5 Total unadjusted error 14
 - 2.2 ADC errors related to its environment 15
 - 2.2.1 Reference voltage noise 15
 - 2.2.2 Reference voltage / power supply regulation 15
 - 2.2.3 External reference voltage parameters 16
 - 2.2.4 Analog input signal noise 16
 - 2.2.5 ADC dynamic range bad match for maximum input signal amplitude . . 16
 - 2.2.6 Effect of the analog signal source resistance 16
 - 2.2.7 Effect of source capacitance and parasitic capacitance of the PCB . . . 17
 - 2.2.8 Injection current effect 18
 - 2.2.9 Temperature influence 18
 - 2.2.10 I/O pin crosstalk 18
 - 2.2.11 EMI-induced noise 19

- 3 **How to get the best ADC accuracy** **20****
 - 3.1 Reduce the effects of ADC-related ADC errors 20
 - 3.2 Minimize ADC errors related to external environment of ADC 20
 - 3.2.1 Reference voltage / Power supply noise minimization 20
 - 3.2.2 Reference voltage / Power-supply regulation 22
 - 3.2.3 Analog-input signal noise elimination 22
 - 3.2.4 Adding white noise or triangular sweep to improve resolution 22
 - 3.2.5 Matching the ADC dynamic range to the maximum signal amplitude . . 23
 - 3.2.6 Analog source resistance calculation 25
 - 3.2.7 Source frequency condition vs. source and parasitic capacitors 27
 - 3.2.8 Temperature-effect compensation 28

3.2.9	Minimizing injection current	28
3.2.10	Minimizing I/O pin crosstalk	28
3.2.11	EMI-induced noise reduction	29
3.2.12	PCB layout recommendations	30
3.2.13	Component placement and routing	31
3.3	Software methods to improve precision	32
3.3.1	Averaging samples	32
3.3.2	Digital signal filtering	32
3.3.3	FFT for AC measurement	33
3.3.4	ADC calibration	34
3.3.5	Minimizing internal CPU noise	34
3.4	High impedance source measurement	35
3.4.1	ADC input stage problem	35
3.4.2	Explanation of the behavior	36
3.4.3	Minimizing added errors	37
3.4.4	Source of described problem - ADC design	41
4	Conclusion	43
5	Revision history	44

List of figures

Figure 1.	Basic schematic of SAR switched-capacitor ADC (example for 10-bit ADC)	5
Figure 2.	Sample state	6
Figure 3.	Hold state	6
Figure 4.	Step 1: Compare with $V_{REF}/2$	7
Figure 5.	Step 2: If MSB = 1, then compare with $\frac{3}{4} V_{REF}$.	7
Figure 6.	Step 2: If MSB = 0, then compare with $\frac{1}{4} V_{REF}$.	8
Figure 7.	Positive offset error representation	10
Figure 8.	Negative offset error representation	10
Figure 9.	Positive gain error representation	11
Figure 10.	Negative gain error representation	11
Figure 11.	Differential linearity error representation	12
Figure 12.	Integral linearity error representation	13
Figure 13.	Total unadjusted error	14
Figure 14.	Input signal amplitude vs. ADC dynamic range	16
Figure 15.	Analog signal source resistance effect	17
Figure 16.	Analog input with R_{AIN} , C_{AIN} and C_p	17
Figure 17.	Effect of injection current	18
Figure 18.	Crosstalk between I/O pins	18
Figure 19.	EMI sources	19
Figure 20.	Power supply and reference decoupling for 100- and 144-pin packages	21
Figure 21.	Power supply decoupling for 36-, 48- and 64-pin packages	21
Figure 22.	Simple quasi-triangular source using a microcontroller output	23
Figure 23.	Selecting the reference voltage	24
Figure 24.	Preamplification	24
Figure 25.	Worst case error: $V_{AIN} = V_{REF+}$	25
Figure 26.	Recommended values for R_{AIN} and C_{AIN} vs. source frequency F_{AIN}	27
Figure 27.	Crosstalk between I/O pins	28
Figure 28.	Shielding technique	29
Figure 29.	Separating the analog and digital layouts	30
Figure 30.	Separating the analog and digital supplies	30
Figure 31.	Typical voltage source connection to ADC input	35
Figure 32.	Noise observed on ADC input pin during ADC conversions	35
Figure 33.	ADC simplified schematic of input stage - sample and hold circuit	36
Figure 34.	ADC input pin noise spikes from internal charge during sampling process	36
Figure 35.	Effect of sampling time extension	37
Figure 36.	Charging the external capacitor with too short time between conversions	38
Figure 37.	Implementation of sampling switch	41
Figure 38.	Parasitic capacitances of sampling switch	41
Figure 39.	Parasitic current example inside ADC structure	42


1 ADC internal principle

1.1 SAR ADC internal structure

The ADC in STM32x microcontrollers uses the *SAR (successive approximation register)* principle, by which the conversion is performed in several steps. The number of conversion steps is equal to the number of bits in the ADC converter. Each step is driven by the ADC clock. Each ADC clock produces one bit from result to output. ADC internal design is a switched-capacitor type.


The following figures (*Figure 1 to Figure 6*) explain the principle of ADC operation. The example given below shows only the first steps of approximation but the process continues till the LSB is reached.

Figure 1. Basic schematic of SAR switched-capacitor ADC (example for 10-bit ADC)

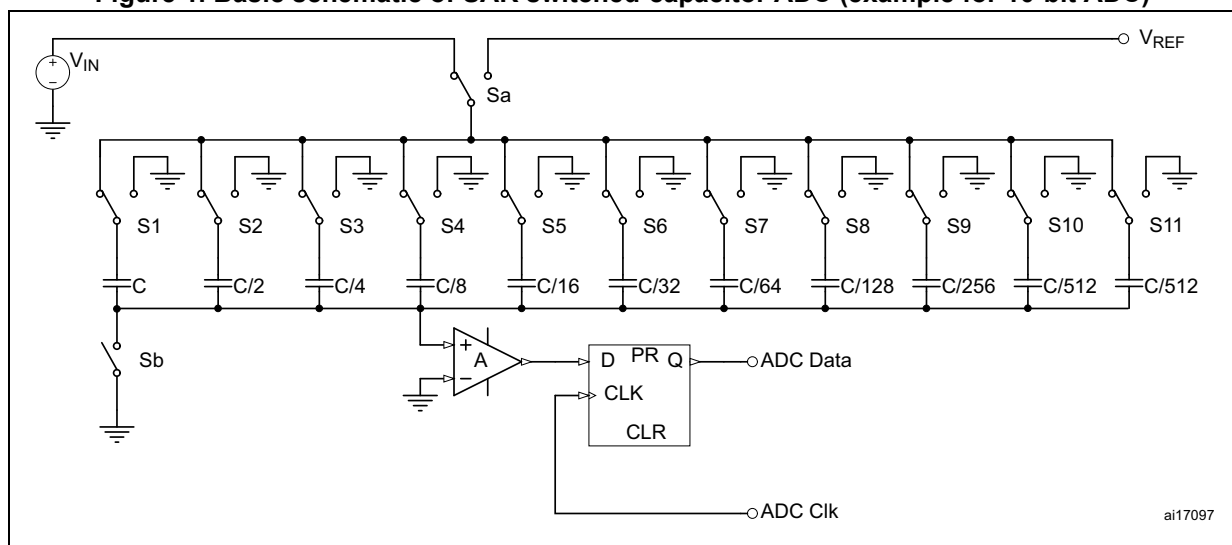


1. Basic ADC schematic with digital output.

Figure 2. Sample state

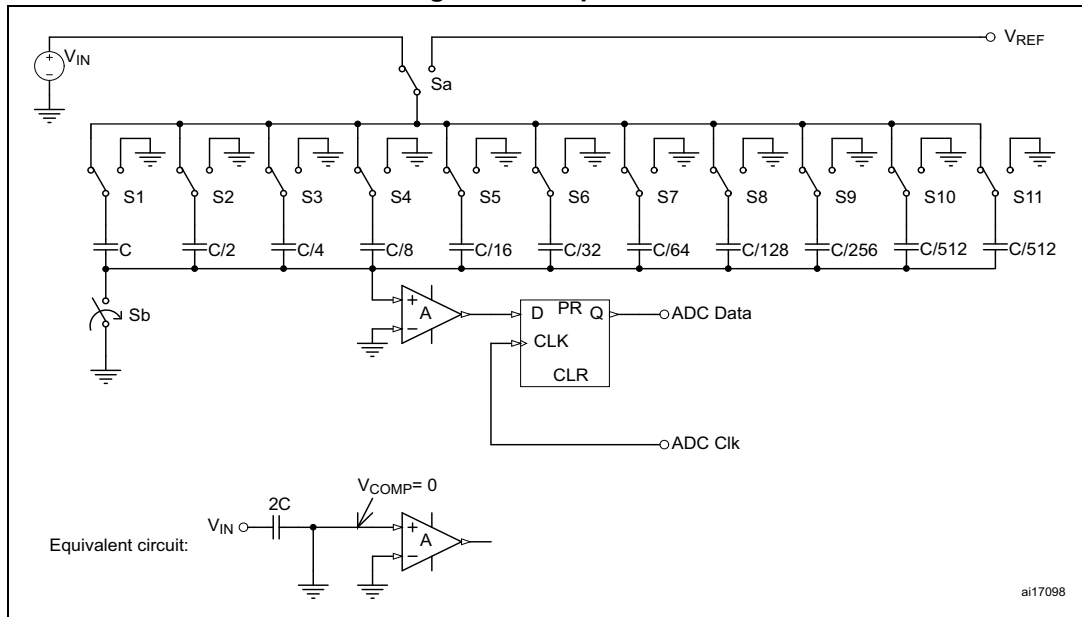


1. Sample state - capacitors are charging to V_{IN} voltage. S_a switch to V_{IN} , S_b switch closed during sampling time.

Figure 3. Hold state

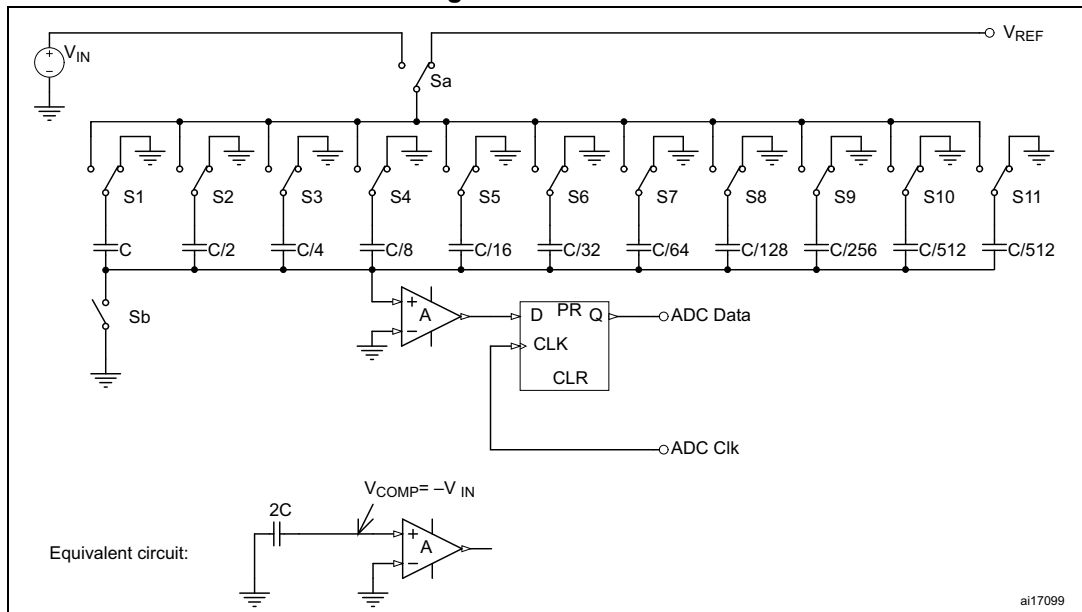


1. Hold state - input is disconnected - capacitors hold input voltage. S_b switch is open, then S_1 - S_{11} switched to ground and S_a switched to V_{REF} .

Figure 4. Step 1: Compare with $V_{REF}/2$

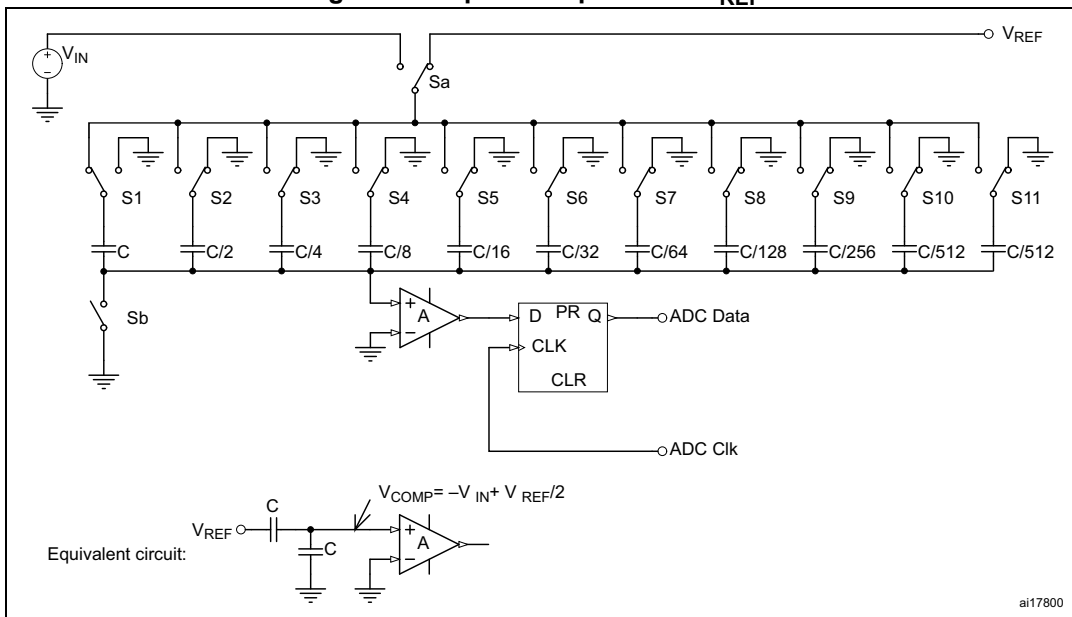


1. First approximation step. S1 switched to V_{REF} .

Figure 5. Step 2: If MSB = 1, then compare with $3/4 V_{REF}$

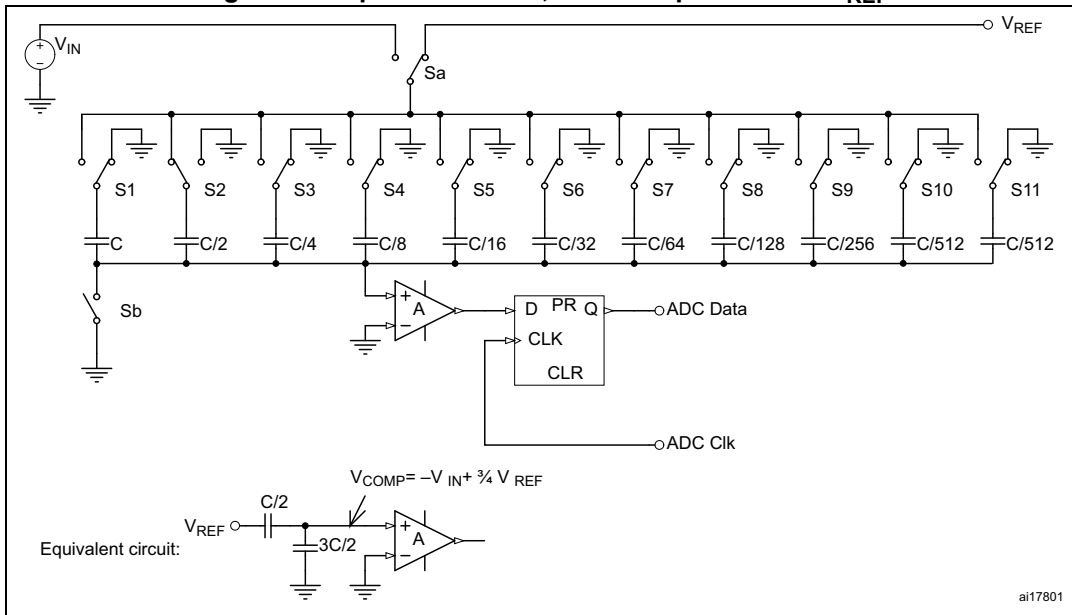

1. Compare with $3/4 V_{REF}$; if MSB = 1. S1 switched back to ground. S2 switched to V_{REF} .

Figure 6. Step 2: If MSB = 0, then compare with $\frac{1}{4} V_{REF}$

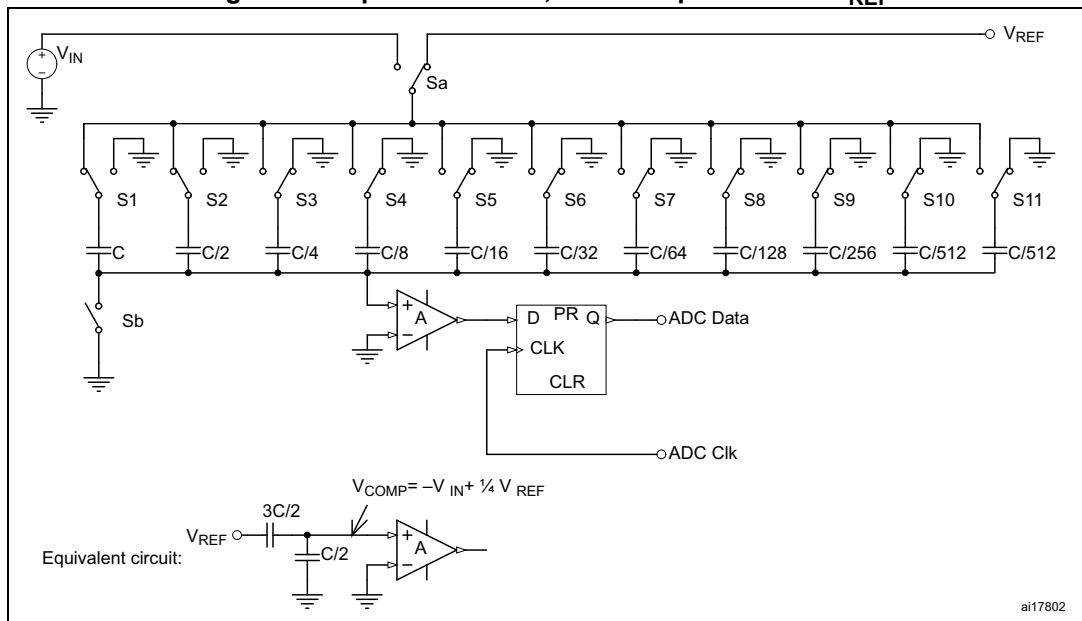

1. Compare with $\frac{1}{4} V_{REF}$; if MSB = 0, S1 remained switched to ground. S2 switched to V_{REF} .

2 ADC errors

This section lists the main errors which have an effect on A/D conversion accuracy. These types of error occur in all A/D converters and conversion quality depends on eliminating them. Values for these errors are specified in the ADC characteristics section of the STM32x device datasheets.

Different accuracy error types are specified for the STM32x ADC. Accuracy errors are normally expressed as multiples of 1 LSB for easy reference. The resolution in terms of voltage depends on the reference voltage. The error in terms of voltage is calculated by multiplying the number of LSBs with the voltage corresponding to 1LSB ($1\text{LSB} = V_{\text{REF+}}/2^{12}$ or $V_{\text{DDA}}/2^{12}$).

2.1 ADC errors related to the ADC itself

2.1.1 Offset error

It is defined as the deviation between the first actual transition and the first ideal transition. The first transition occurs when the digital output of the ADC changes from 0 to 1. Ideally, when the analog input is between 0.5 LSB and 1.5LSB, the digital output should be 1. Ideally still, the first transition occurs at 0.5 LSB. The offset error is denoted by E_{O} . Offset error can easily be calibrated by the application firmware.

Example

For the STM32x ADC, the smallest detectable incremental change in voltage is expressed in terms of LSBs:

$$1 \text{ LSB} = V_{\text{REF+}}/4096 \text{ (on some packages is } V_{\text{REF+}} = V_{\text{DDA}}\text{)}$$

If $V_{\text{REF+}} = 3.3 \text{ V}$, ideally, the input of $402.8 \mu\text{V}$ ($0.5 \text{ LSB} = 0.5 \times 805.6 \mu\text{V}$) should lead to the generation of a digital output of 1. In practice, however, the ADC may still show the reading as 0. If a digital output of 1 is obtained from an analog input of $550 \mu\text{V}$, then:


$$\text{Offset error} = \text{Actual transition} - \text{Ideal transition}$$

$$E_{\text{O}} = 550 \mu\text{V} - 402.8 \mu\text{V} = 141.2 \mu\text{V}$$

$$E_{\text{O}} = 141.2 \mu\text{V} / 805.6 \mu\text{V} = 0.17 \text{ LSB}$$

When an analog input voltage greater than 0.5LSB generates the first transition, the offset error is positive. [Figure 7](#) shows a positive offset error.


Figure 7. Positive offset error representation

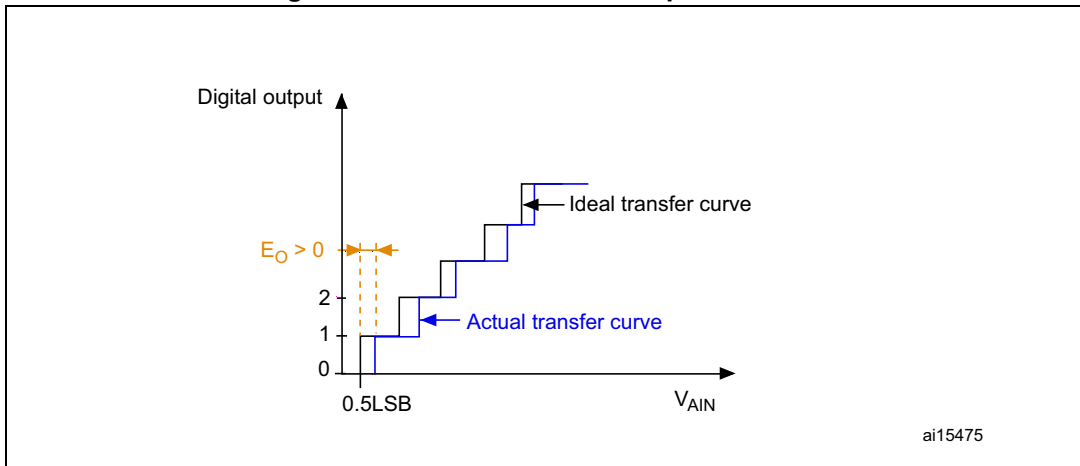

When an analog input voltage of less than 0.5LSB generates the first transition, the offset error is negative. [Figure 8](#) shows a negative offset error.

If the analog input voltage $V_{AIN} = V_{SSA}$ and the ADC generates a nonzero digital output, the offset error is negative. This means that a negative voltage generates the first transition.

Figure 8. Negative offset error representation

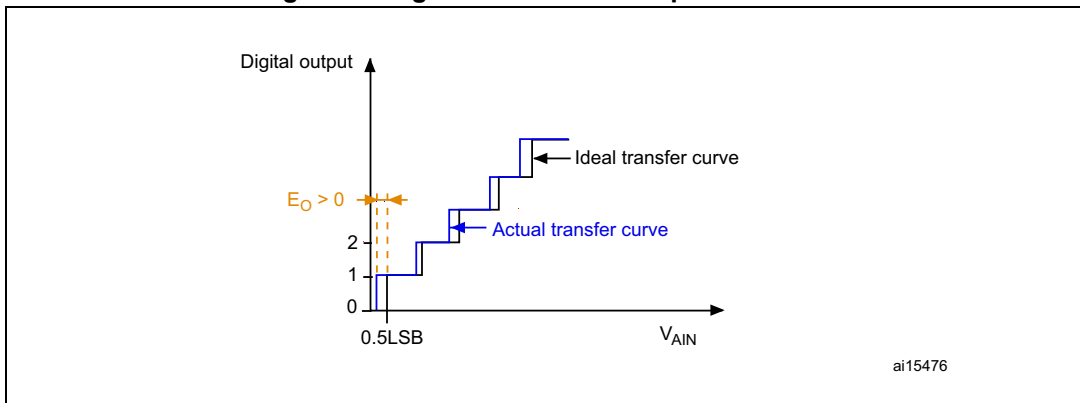

2.1.2 Gain error

Gain error is defined as the deviation between the last actual transition and the last ideal transition. Gain error is represented as E_G

The last actual transition is the transition from FFEh to FFFh. Ideally, there should be a transition from FFEh to FFFh, when the analog input is equal to $V_{REF+} - 0.5LSB$. So for $V_{REF+} = 3.3$ V, the last ideal transition should be at 3.299597 V.

If the ADC provides the FFFh reading for $V_{AIN} < V_{REF+} - 0.5LSB$, then we have a negative gain error.

Example

Gain error $E_G = \text{Last actual transition} - \text{ideal transition}$

If $V_{REF+} = 3.3$ V and $V_{AIN} = 3.298435$ V generates a transition from FFE to FFF then,

$$E_G = 3.298435 \text{ V} - 3.299597 \text{ V}$$

$$E_G = -1162 \text{ } \mu\text{V}$$

$$E_G = (-1162 \text{ } \mu\text{V} / 805.6 \text{ } \mu\text{V}) \text{ LSB} = -1.44 \text{ LSB}$$

If we do not get a full scale reading (FFFh) for V_{AIN} equal to V_{REF+} , the gain error is positive. This means that a voltage greater than V_{REF+} will cause the last transition. [Figure 9](#) shows a positive gain error and [Figure 10](#), a negative gain error.

Figure 9. Positive gain error representation


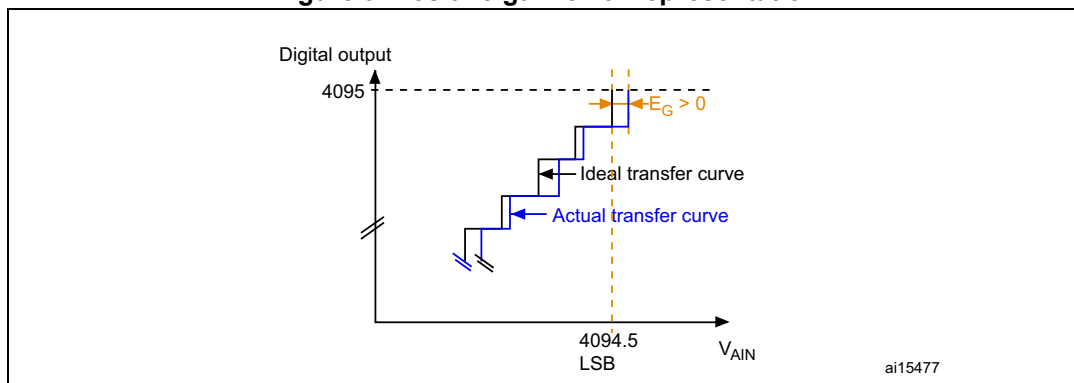


Figure 10. Negative gain error representation

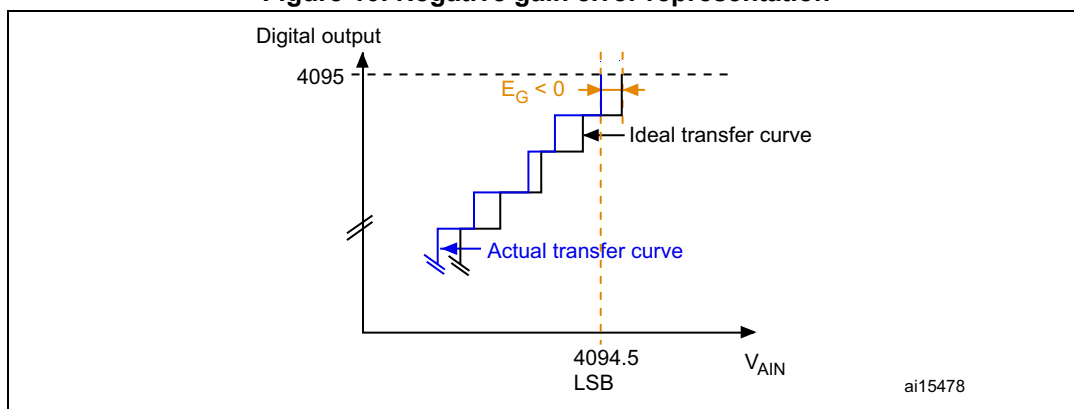

2.1.3 Differential linearity error

The differential linearity error (DLE) is defined as the maximum deviation between the actual and ideal steps. Here 'ideal' is not used for the ideal transfer curve but for the resolution of the ADC. The DLE is denoted by E_D . It is represented in [Figure 11](#).

$$E_D = \text{Actual step width} - 1\text{LSB}$$


Ideally, an analog input voltage change of 1LSB should cause a change in the digital code. If an analog input voltage greater than 1LSB is required for a change in digital code, the ADC has a differential linearity error. The DLE therefore corresponds to the maximum additional voltage that is required to change from one digital code to the next.

The DLE is also known as the differential non-linearity (DNL) error.

Example

A given digital output should correspond to an analog input range. Ideally, the step width should be 1LSB. Let us assume that we get the same digital output over an analog input voltage range of 1.9998 V to 2.0014 V, the step width will be $2.0014 \text{ V} - 1.9998 \text{ V} = 1.6 \text{ mV}$. E_D is thus the voltage difference between the higher (2.0014 V) and lower (1.9998 V) analog voltages less the voltage corresponding to 1LSB.

Figure 11. Differential linearity error representation

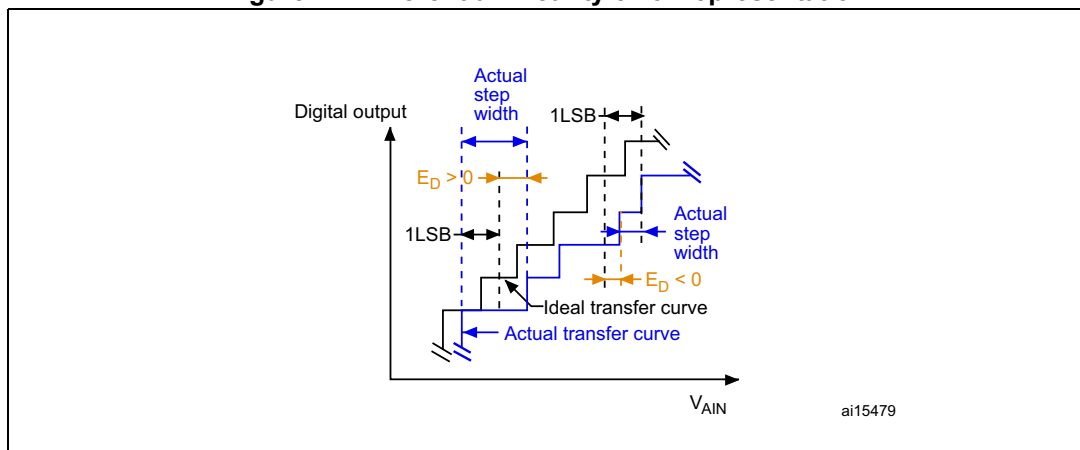

If $V_{REF+} = 3.3 \text{ V}$, an analog input of 1.9998 V (9B1h) can provide results varying between 9B0h and 9B2h. Similarly, for an input of 2.0014 V (9B3h), the results may vary between 9B2h and 9B4h.

Thus, the total voltage variation corresponding to the 9B2h step is:

$$9B3h - 9B1h, \text{ that is, } 2.0014 \text{ V} - 1.9998 \text{ V} = 1.6 \text{ mV} (1660 \mu\text{V})$$

$$E_D = 1660 \mu\text{V} - 805.6 \mu\text{V}$$

$$E_D = 854.4 \mu\text{V}$$

$$E_D = (854.4 \mu\text{V} / 805.6 \mu\text{V}) \text{ LSB}$$

$$E_D = 1.06 \text{ LSB}$$

Let us assume that no voltage greater than 2.0014 V will result in the 9B2h digital code. When the step width is less than 1LSB, E_D is negative.


2.1.4 Integral linearity error

The integral linearity error is the maximum deviation between any actual transition and the endpoint correlation line. The ILE is denoted by E_L . It is represented in [Figure 12](#).

The endpoint correlation line can be defined as the line on the A/D transfer curve that connects the first actual transition with the last actual transition. E_L is the deviation from this line for each transition. The endpoint correlation line thus corresponds to the actual transfer curve and has no relation to the ideal transfer curve.

The ILE is also known as the integral non linearity error (INL). The ILE is the integral of the DLE over the whole range.

Figure 12. Integral linearity error representation

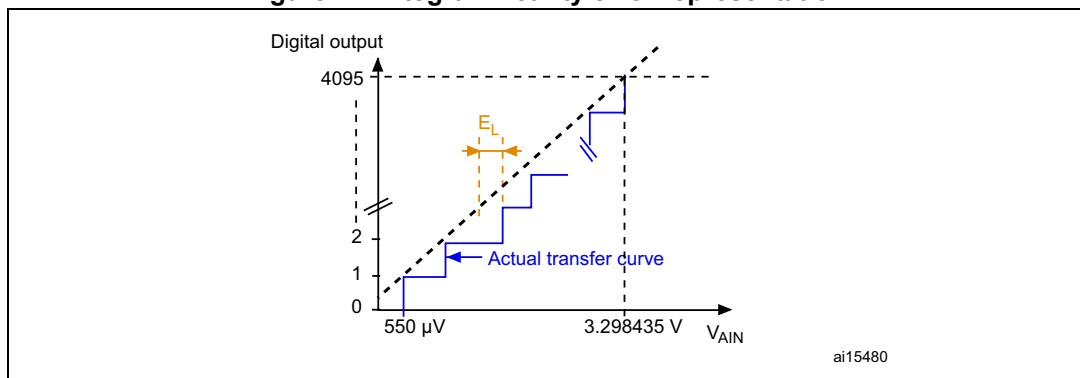

Example

If the first transition from 0 to 1 occurs at $550 \mu\text{V}$ and the last transition (FFEh to FFFh) occurs at 3.298435 V (gain error), then the line on the transfer curve connecting the actual digital codes 1h and FFFh will be the endpoint correlation line.

2.1.5 Total unadjusted error

The total unadjusted error (TUE) is defined as the maximum deviation between the actual and the ideal transfer curves. It is a parameter that specifies the total errors that may occur, causing maximum deviation between the ideal digital output and the actual digital output. It is the maximum deviation recorded between the ideal expected value and the actual value obtained from the ADC for any input voltage.

The TUE is denoted by E_T . It is represented in *Figure 13*.


The TUE is not the sum of E_O , E_G , E_L , E_D . The offset error affects the digital result at lower voltages whereas the gain error affects the digital output for higher voltages.

Example

If $V_{REF+} = 3.3\text{ V}$ and $V_{AIN} = 2\text{ V}$, the ideal result is 9B2h. But if, on conversion, we get the result 9B4h, the deviation may result from the offset since the DLE and ILE errors occur simultaneously.

$$TUE = \text{absolute (actual value - ideal case value)} = 9B4h - 9B2h = 2h = 2\text{LSB}$$

Figure 13. Total unadjusted error

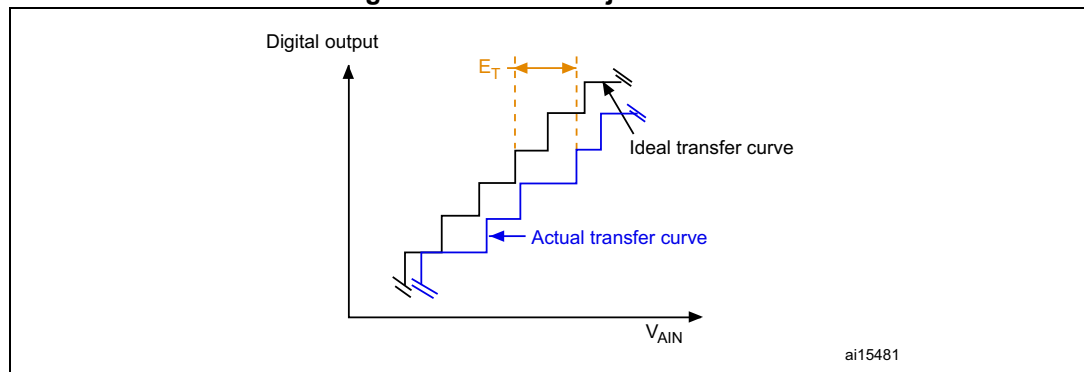

2.2 ADC errors related to its environment

2.2.1 Reference voltage noise

As the ADC output is the ratio between the analog signal voltage and the reference voltage, any noise on the analog reference will cause a change in the converted digital value. The V_{DDA} analog power supply is used on some packages as the reference voltage (V_{REF+}) so the quality of this power supply has influence to ADC error.

For example, with an analog reference of 3.3 V ($V_{REF+} = V_{DDA}$) and a 1 V signal input, the converted result is $(1/3.3) \times 4095 = 4D9h$

But with a 40 mV peak-to-peak ripple in the analog reference, the converted value becomes $(1/3.34) \times 4095 = 4CAh$ (with V_{REF+} at its peak).

Error = $4D9 - 4CA = 15$ LSB

The SMPS (switch-mode power supply) normally has internal fast-switching power transistors. This introduces high-frequency noise in the output. The switching noise is in the range of 15 kHz to 1 MHz.

2.2.2 Reference voltage / power supply regulation

Power supply regulation is very important for ADC accuracy since the conversion result is the ratio of the analog input voltage to the V_{REF+} value.

If the power supply output decreases when connected to V_{DDA} or V_{REF+} due to the loads on these inputs and to its output impedance, an error will be introduced in the conversion result.

Digital code = $\frac{V_{AIN}(2^N - 1)}{V_{REF+}}$, where N is the resolution of the ADC (in our case N = 12).

If the reference voltage changes, the digital result changes too.

For example:

If the supply used is a reference voltage of 3.3 V and $V_{AIN} = 1$ V, the digital output is:

$$\text{Digital}_{\text{output}} = \frac{1 \times (2^{12} - 1)}{3.3} = 4D9h$$

If the voltage supply provides a voltage equal to 3.292 V (after its output connection to V_{REF+}), then:

$$\text{Digital}_{\text{output}} = \frac{1 \times (2^{12} - 1)}{3.292} = 4DCh$$

The error introduced by the voltage drop is: $4DC - 4D9 = 3$ LSB .

2.2.3 External reference voltage parameters

In case of usage external source for reference voltage (on V_{REF+} pin) there are important parameters of this external reference source. It is important to look at three reference voltage specifications: temperature drift, voltage noise, long term stability.

2.2.4 Analog input signal noise


Small but high-frequency signal variation can result in big conversion errors during sampling time. This noise is generated by electrical devices, for example, motors, engine ignition, power lines, and so on, and affects the source signal (for example a sensor) by adding an unwanted signal. As a consequence, the conversion results of the ADC are not accurate.

2.2.5 ADC dynamic range bad match for maximum input signal amplitude

It is very important that the ADC dynamic range matches the maximum amplitude of the signal to be converted to have the maximum ADC conversion precision. Let us assume that the signal to be converted varies between 0 V to 2.5 V and that V_{REF+} is equal to 3.3 V. The maximum signal value converted by the ADC is 3102 (2.5 V) as shown in [Figure 14](#). In this case, there are 993 unused transitions (4095 – 3102 = 993). This implies a loss in the converted signal accuracy.

See [Section 3.2.5: Matching the ADC dynamic range to the maximum signal amplitude on page 23](#) for details on how to have the ADC dynamic range matching the maximum input signal amplitude.

Figure 14. Input signal amplitude vs. ADC dynamic range

 


2.2.6 Effect of the analog signal source resistance

The impedance of the analog signal source, or series resistance (R_{AIN}), between the source and pin causes a voltage drop across it because of the current flowing into the pin. The charging of the internal sampling capacitor C_{ADC} is controlled by switches with resistance R_{ADC} .

With the addition of source resistance (with R_{ADC}), the time required to fully charge the hold capacitor increases. [Figure 15](#) shows the analog signal source resistance effect.

The effective charging of C_{ADC} is governed by $R_{ADC} + R_{AIN}$, so the charging time constant becomes $t_c = (R_{ADC} + R_{AIN}) \times C_{ADC}$. If the sampling time is less than the time required to fully charge the C_{ADC} through $R_{ADC} + R_{AIN}$ ($t_s < t_c$), the digital value converted by the ADC is less than the actual value.

Figure 15. Analog signal source resistance effect

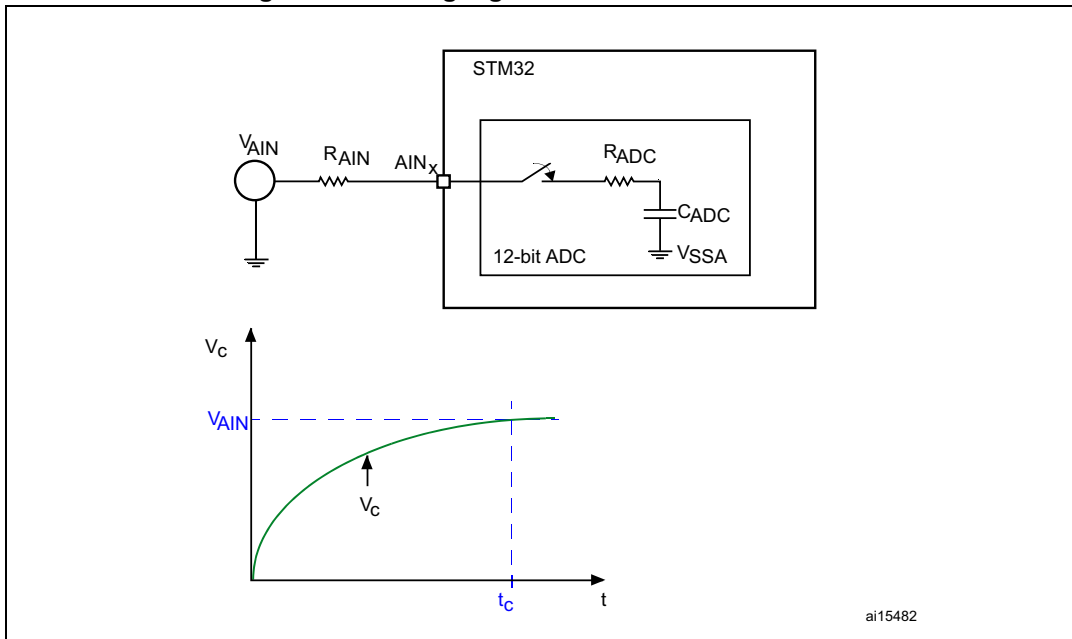


1. t_c is the time taken by the C_{ADC} capacitor to fully charge: $V_c = V_{AIN}$ (with max. 1/2 lsb error)
 V_c : capacitor (C_{ADC}) voltage
 $t_c = (R_{ADC} + R_{AIN}) \times C_{ADC}$

2.2.7 Effect of source capacitance and parasitic capacitance of the PCB

When converting analog signals, it is necessary to account for the capacitance at the source and the parasitic capacitance seen on the analog input pin (refer to Figure 16). The source resistance and capacitance form an RC network and the ADC conversion results may not be accurate unless the external capacitor ($C_{AIN} + C_p$) is fully charged to the level of the input voltage. The greater value of ($C_{AIN} + C_p$), the more limited the source frequency.

The external capacitance at the source and the parasitic capacitance are denoted by C_{AIN} and C_p , respectively.


Figure 16. Analog input with R_{AIN} , C_{AIN} and C_p

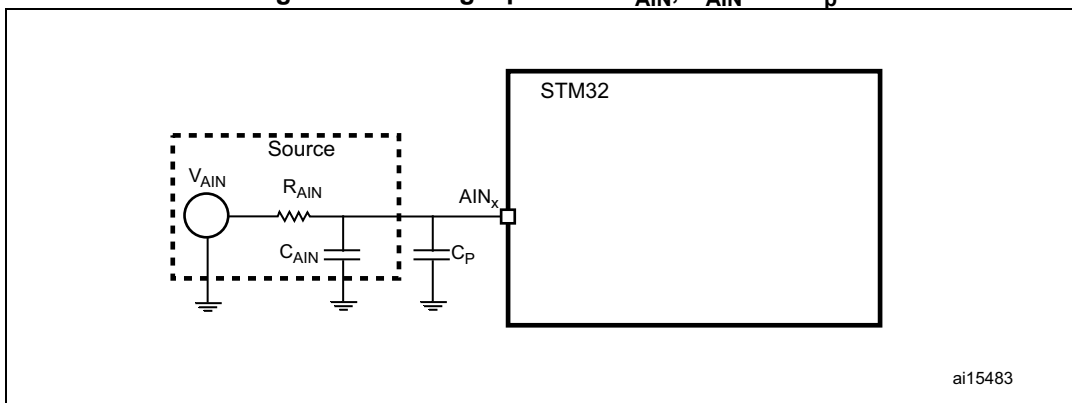

2.2.8 Injection current effect

A negative injection current on any analog pin (or a closely positioned digital input pin) may introduce leakage current into the ADC input. The worst case is the adjacent analog channel. A negative injection current is introduced when $V_{AIN} < V_{SS}$, causing current to flow out from the I/O pin. This is illustrated in [Figure 17](#).

Figure 17. Effect of injection current

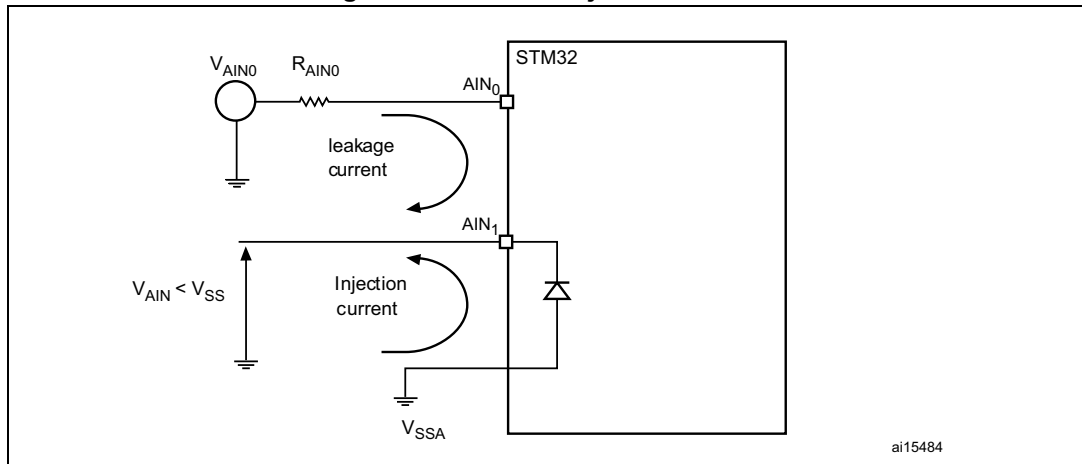

2.2.9 Temperature influence


The temperature has a major influence on ADC accuracy. Mainly it leads to two major errors: offset error drift and gain error drift. Those errors can be compensated in the microcontroller firmware (refer to [Section 3.2.8](#) for the temperature-compensation methods).

2.2.10 I/O pin crosstalk

Switching the I/Os may induce some noise in the analog input of the ADC due to capacitive coupling between I/Os. Crosstalk may be introduced by PCB tracks that run close to each other or that cross each other.

Internally switching digital signals and I/Os introduces high-frequency noise. Switching high-sink I/Os may induce some voltage dips in the power supply caused by current surges. A digital track that crosses an analog input track on the PCB may affect the analog signal (see [Figure 18](#)).

Figure 18. Crosstalk between I/O pins

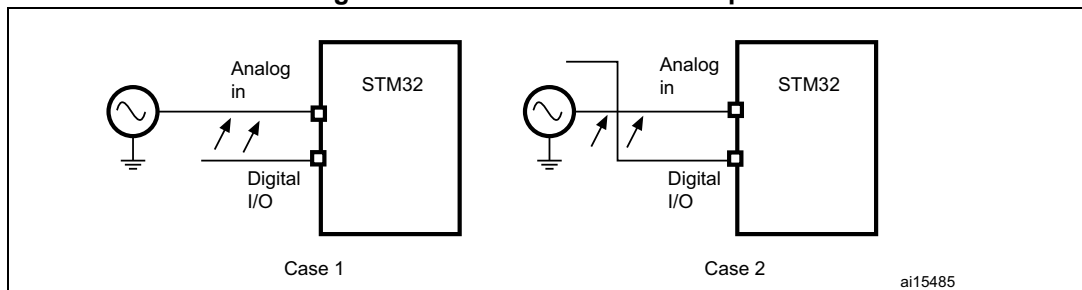


Case 1: Digital and analog signal tracks that pass close to each other.

Case 2: Digital and analog signal tracks that cross each other on a different PCB side.

2.2.11 EMI-induced noise

Electromagnetic emissions from neighboring circuits may introduce high-frequency noise in an analog signal because the PCB tracks may act like an antenna (See [Figure 19](#)).

Figure 19. EMI sources

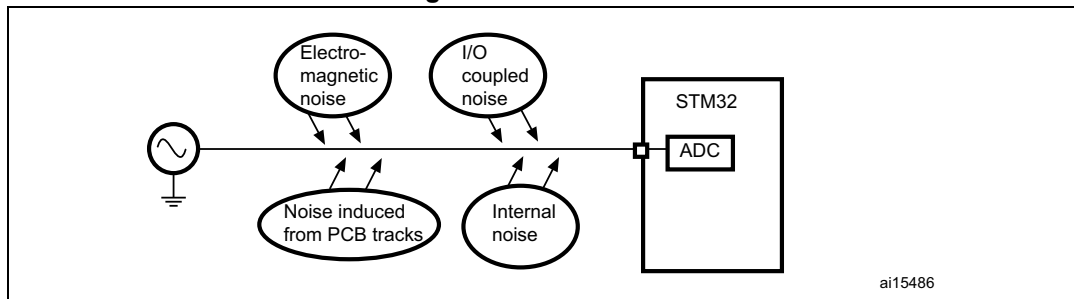

3 How to get the best ADC accuracy

3.1 Reduce the effects of ADC-related ADC errors

The TUE is not the sum of all the errors E_O , E_G , E_L , E_D . It is the maximum deviation that can occur between the ideal and actual digital values. It can result from one or more errors occurring simultaneously.

As the ILE is the integral of the DLE, it can be considered as the indicator of the maximum error. Do not add the DLE and ILE together to calculate the maximum error that may occur at any digital step.

The maximum error values specified in the datasheet are the worst error values measured in laboratory test environment over the given voltage and temperature range (see device datasheet).

The ILE and DLE are dependent on the ADC design. It is difficult to calibrate them. They can be calibrated by the measured ADC curve stored in the microcontroller memory but this needs calibration of each individual device in final application.

Offset and gain errors can be easily compensated using the STM32x ADC self-calibration feature or by microcontroller firmware.

3.2 Minimize ADC errors related to external environment of ADC

3.2.1 Reference voltage / Power supply noise minimization

Power supply side

Linear regulators have a better output in terms of noise. The mains must be stepped down, rectified and filtered, then fed to linear regulators. It is highly recommended to connect the filter capacitors to the rectifier output. Please refer to the datasheet of the used linear regulator.

If you are using a switching power supply, it is recommended to have a linear regulator to supply the analog stage.

It is recommended to connect capacitors with good high-frequency characteristics between the power and ground lines. That is, a 0.1 μF and a 1 to 10 μF capacitor should be placed close to the power source.

The capacitors allow the AC signals to pass through them. The small-value capacitors filter high-frequency noise and the high-value capacitors filter low-frequency noise. Ceramic capacitors are generally available in small values (1 pF to 0.1 μF) and with small voltage ratings (16 V to 50 V). It is recommended to place them close to the main supply (V_{DD} and V_{SS}) and analog supply (V_{DDA} and V_{SSA}) pins. They filter the noise induced in the PCB tracks. Small capacitors can react fast to current surges and discharge quickly for fast-current requirements.

Tantalum capacitors can also be used along with ceramic capacitors. To filter low-frequency noise, you can use high-value capacitors (10 μF to 100 μF), which are generally electrolytic. It is recommended to put them near the power source.

To filter high-frequency noise, you can use a ferrite inductance in series with the power supply. This solution leads to very low (negligible) DC loss unless the current is high

because the series resistance of the wire is very low. At high frequencies, however, the impedance is high.

STM32x side

In most STM32x microcontrollers the V_{DD} and V_{SS} pins are placed close to each other. So are the V_{REF+} and V_{SSA} pins. A capacitor can therefore be connected very close to the microcontroller with very short leads. For multiple V_{DD} and V_{SS} pins, use separate decoupling capacitors.

The V_{DDA} pin must be connected to two external decoupling capacitors (10 nF Ceramic + 1 μ F Tantalum or Ceramic). See [Figure 20](#) and [Figure 21](#) for decoupling examples.

For STM32x devices delivered in 100/144-pin packages, it is possible to improve the accuracy on low-voltage inputs by connecting a separate external ADC reference voltage input on V_{REF+} (refer to [Section 3.2.5](#)). The voltage on V_{REF+} may range from 2.4 V to V_{DDA} . If a separate, external reference voltage is applied on V_{REF+} , two 10 nF and 1 μ F capacitors must be connected on this pin. In all cases, V_{REF+} must be kept between 2.4 V and V_{DDA} .

Figure 20. Power supply and reference decoupling for 100- and 144-pin packages


 


Figure 21. Power supply decoupling for 36-, 48- and 64-pin packages

 

3.2.2 Reference voltage / Power-supply regulation

The power supply should have good line and load regulation since the ADC uses V_{REF+} or V_{DDA} as the analog reference and the digital value is the ratio of the analog input signal to this voltage reference. V_{REF+} must thus remain stable at different loads.

Whenever the load is increased by switching on a part of the circuit, the increase in current must not cause the voltage to decrease. If the voltage remains stable over a wide current range, the power supply has good load regulation.

For example: for the LD1086D2M33 voltage regulator, the line regulation is 0.035% typical when V_{IN} varies from 2.8 V to 16.5 V (when $I_{load} = 10$ mA), and the load regulation is 0.2% when I_{load} varies from 0 to 1.5 A (please refer to the LD1086 series datasheet for details).

The lower the line regulation value, the better the regulation. Similarly, the lower the load regulation value, the better the regulation and the stability of the voltage output.

It is also possible to use a reference voltage for V_{REF+} , for instance the LM236, which is a voltage reference diode of 2.5 V (refer to LM236 datasheet for more details).

3.2.3 Analog-input signal noise elimination

Averaging method

Averaging is a simple technique where you sample an analog input several times and take the average of the results by software. This technique is helpful to eliminate the effect of noise on the analog input in case of an analog voltage that does not change often.

The average has to be made on several readings that all correspond to the same analog input voltage. Make sure that the analog input remains at the same voltage during the time period when the conversions are done, otherwise you will add up digital values corresponding to different analog inputs, and you will introduce errors.

Adding an external filter

Adding an external RC filter eliminates the high frequency. An expensive filter is not needed to deal with a signal that has frequency components above the frequency range of interest. In this case, a relatively simple lowpass filter with a cutoff frequency f_C just above the frequency range of interest will suffice to limit noise and aliasing. A sampling rate consistent with the highest frequency of interest will suffice, typically 2 to 5 times f_C .

Note: The R and C that form the external filter should have values that match the conditions described in [Section 3.2.4](#) and [Section 3.2.7](#).

3.2.4 Adding white noise or triangular sweep to improve resolution

This method combines hardware and software techniques to improve precision. From a software point of view, this method uses averaging (oversampling) and from a hardware point of view, it uses signal modification/spreading/dithering.


Averaging can be used in cases where the input signal is noisy (some signal change is necessary in order to be able to calculate an average) and the requirement is to obtain the mean value of a signal. A problem appears when the input signal is a very stable voltage without noise. In this case, when the input signal is measured, each data sample is the same. This is because the input signal level is somewhere between two ADC word levels (e.g. between 0x14A and 0x14B). Therefore it is not possible to determine the input voltage level more precisely (e.g. if the level is near to 0x14A or near to 0x14B level).

The solution is to add noise or some signal change (with uniform signal distribution e.g. triangular sweep) to the input signal which pushes its level across 1-bit ADC level (so that the signal level changes below 0x14A and above 0x14B level). This causes the ADC results to vary. Applying software averaging to the different ADC results, produces the mean value of the original input signal.

Example of implementation of this method is done by using a triangular generator with RC coupling to the input signal (white noise generation is more complicated). Care must be taken not to modify the mean value of the original input signal (so, capacitive coupling must be used).

A very simple implementation of the quasi-triangular source which is generated directly by the STM32x microcontroller is on [Figure 22](#).

Figure 22. Simple quasi-triangular source using a microcontroller output

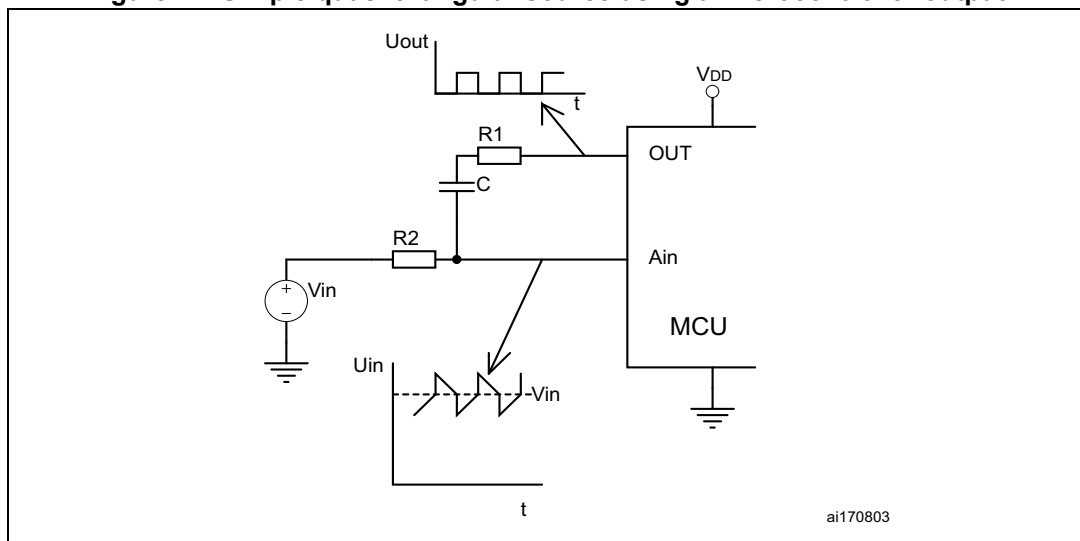

3.2.5 Matching the ADC dynamic range to the maximum signal amplitude

This method improves accuracy by a proper selection of the reference voltage or by using a preamplifier stage to obtain the maximum possible resolution using the full ADC output range.

Selecting a reference voltage (method for devices delivered in 100-/144-pin packages only)


The reference voltage is selected in the expected range of the signal to be measured. If the measured signal has an offset, then the reference voltage should also have a similar offset. If the measured signal has a defined maximum amplitude, then the reference voltage should also have a similar maximum value. By matching this reference voltage to the measurement signal range, we obtain the maximum possible resolution using the full ADC output range.

In STM32x devices delivered in 100- and 144-pin packages, the ADC reference voltage is connected to the external V_{REF+} and V_{REF-} pins that should be tied to ground. This makes it possible to match the reference voltage and the measured signal range.

For example, if the measured signal varies between 0 V and 2.5 V, it is recommended to choose $V_{REF+} = 2.5$ V, possibly using a reference voltage like LM235 (see LM235 datasheet for more details). [Figure 23](#) illustrates these conditions.

Note: The voltage on V_{REF+} may range between 2.4 V and V_{DDA} .

Figure 23. Selecting the reference voltage

 


Using a preamplifier

If the measured signal is too small (in comparison with the ADC range) then it is good to use an external preamplifier. This method can be implemented with STM32x devices delivered in all packages, and more specifically so in packages that do not have the V_{REF+} input.

For example, if the measured signal varies between 0 V to 1 V and V_{DDA} is 3 V, the signal can be amplified so that its peak-to-peak amplitude is similar to the V_{DDA} value. The gain will then be equal to 3. Figure 24 illustrates this example.

This amplifier can adapt the input signal range to the ADC range. It can also insert offsets between the input signal and the ADC input. Care must be taken in the preamplifier design not to generate additional errors (for example additional offset, amplifier gain stability, linearity, frequency response, etc.).

Figure 24. Preamplification

 


3.2.6 Analog source resistance calculation

Let us assume that the maximum error allowed is equal to 1/2 LSB. We will calculate the maximum source resistance allowed.

V_C is the voltage across the internal C_{ADC} capacitor (refer to [Figure 15](#)).

Then we have: $\text{Error} = V_{AIN} - V_C = \frac{1}{2}\text{LSB}$

Figure 25. Worst case error: $V_{AIN} = V_{REF+}$

 

Let t_s be the sampling time.

$$t_s = T_S/f_{ADC}, \text{ where } T_S \text{ is the sampling time evaluated by cycles} \quad (1)$$

For a given t_s , the error corresponding to $V_{AIN} = V_{REF+}$ is greater than the error corresponding to $V_{AIN} < V_{REF+}$ because the C_{ADC} capacitor takes more time to charge from 0 V to V_{AIN} when $V_{AIN} = V_{REF+}$ than it takes when $V_{AIN} < V_{REF+}$ (refer to [Figure 25](#)). So $V_{AIN} = V_{REF+}$ is the worst case to be taken into account in the demonstration of the maximum source resistance.

$$\text{Error} = V_{REF+} - V_{REF+} \left(1 - e^{-\frac{t_s}{R_{\max} C_{ADC}}} \right) = \frac{1}{2} \cdot \frac{V_{REF+}}{2^N}, \text{ where:}$$

- $R_{\max} = (R_{AIN} + R_{ADC})_{\max}$ (2)
- N is the ADC resolution (in our case $N = 12$)

$$\text{This gives: } e^{-\frac{t_s}{R_{\max} C_{ADC}}} = \frac{1}{2^{N+1}}. \text{ Thus: } R_{\max} = \frac{t_s}{C_{ADC} \cdot \ln(2^{N+1})} \quad (3)$$

By combining equations (1), (2) and (3), we obtain final formula:

$$R_{AIN\max} = \frac{T_S}{f_{ADC} \cdot C_{ADC} \cdot \ln(2^{N+1})} - R_{ADC\max}$$

Example for STM32F1 parameters:

$f_{ADC} = 14 \text{ MHz}$, $C_{ADC} = 8 \text{ pF}$, $R_{ADCmax} = 1 \text{ k}\Omega$ and for $T_s = 7.5$, the maximum source resistance allowed for an error equal to 1/2 LSB is:

$$R_{AINmax} = \frac{7.5}{14 \cdot 10^6 \cdot 8 \cdot 10^{-12} \cdot \ln(2^{12} + 1)} - 1 \text{ k}\Omega$$

That is:

$$R_{AINmax} = 6.4 \text{ k}\Omega$$

Note: The use of a follower amplifier can reduce the resistance of the source effect because of its high input impedance and its very low output impedance. It isolates R_{AIN} from R_{ADC} . However, the amplifier introduces an offset error that should be taken into account.

In case of longer sampling times and reduced number of ADC clocks, better results can be obtained. It is possible to further increase the allowed external resistance by decreasing the ADC clock frequency or selecting a lower resolution. Refer to the datasheet of your device to obtain the exact values of the RC parameters.

3.2.7 Source frequency condition vs. source and parasitic capacitors

The external capacitance will not allow the analog input voltage to be exactly the same as V_{AIN} if the capacitor is not fully charged by the analog source.

If the analog input signal changes, then the analog signal frequency (F_{AIN}) should be such that the time period of this analog signal is at least: $10 \times R_{AIN} \times (C_{AIN} + C_p)$.

T_{AIN} = analog signal time period = $1/F_{AIN}$.

We have: $T_{AIN} \geq 10 \times R_{AIN} \times (C_{AIN} + C_p)$

Therefore: $F_{AIN} \leq \frac{1}{10 \times R_{AIN} \times (C_{AIN} + C_p)}$

For example:


For $R_{AIN} = 25 \text{ k}\Omega$, $C_{AIN} = 7 \text{ pF}$, $C_p = 3 \text{ pF}$, this gives:

$$F_{AINmax} = \frac{1}{10 \times 25 \times 10^3 \times (7 + 3) \times 10^{-12}}$$

Thus, the maximum frequency of the source will be: $F_{AINmax} = 400 \text{ kHz}$.

So for the above defined source characteristics (capacitance and resistance), the frequency of the source must not exceed 400 kHz, otherwise the ADC conversion result will be not accurate.

Figure 26. Recommended values for R_{AIN} and C_{AIN} vs. source frequency F_{AIN}

 

3.2.8 Temperature-effect compensation

One method would be to fully characterize the offset and gain drift and provide a lookup table in memory to correct measurement according to temperature change. This calibration involves additional cost and takes time.

The second method consists in recalibrating the ADC when the temperature change reaches given values, by using the internal temperature sensor and the ADC watchdog.

3.2.9 Minimizing injection current

Check the application to verify whether any digital or analog input voltage can be less than V_{SS} or V_{SSA} . If it is the case, a negative injection current will flow from the pins. The effect on the accuracy will be greater if a digital input is close to the analog input being converted.

Negative current injection on any of the standard (non-robust) analog input pins should be avoided as this would significantly reduce the accuracy of the conversion being performed on another analog input.


It is recommended to connect a Schottky diode between V_{SSA} and the I/O pin that can give birth to the negative injection current.

The ADC accuracy will not be affected by positive injection currents within the limits specified for $I_{INJ(PIN)}$ and $\Sigma I_{INJ(PIN)}$ (refer to the appropriate STM32x datasheet, I/O port characteristics section).

3.2.10 Minimizing I/O pin crosstalk

The noise produced by crosstalk can be reduced by shielding the analog signal by placing ground tracks across it. [Figure 27](#) shows the recommended grounding between signals.

Figure 27. Crosstalk between I/O pins

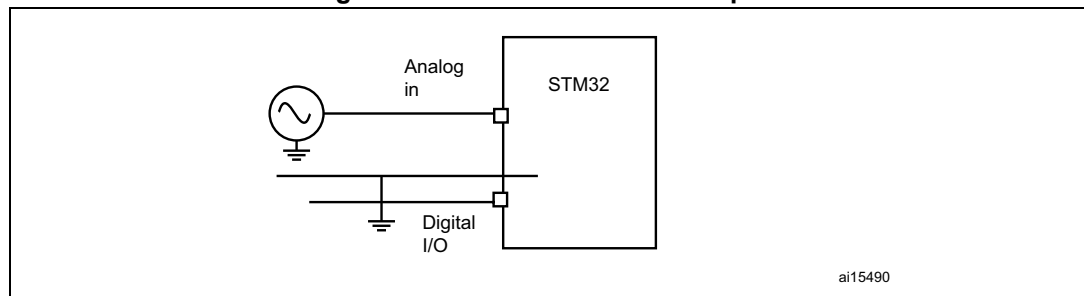

3.2.11 EMI-induced noise reduction

You can reduce EMI noise using proper shielding and layout techniques. The possible sources of emission must be physically separated from the receptors. They can be separated electrically by proper grounding and shielding.

Shielding technique


Placing ground tracks alongside sensitive analog signals provides shielding on the PCB. The other side of the two-layer PCB should also have a ground plane. This prevents interference and I/O crosstalk affecting the signal. See [Figure 28](#).

Signals coming from distant locations (like sensors, etc.) should be connected to the PCB using shielded cable. Care should be taken to minimize the length of the paths of these types of signal on the PCB.

The shield should not be used to carry the ground reference from the sensor or analog source to the microcontroller. A separate wire should be used as ground. The shield should be grounded at only one place near the receiver such as the analog ground of the microcontroller. Grounding the shield at both ends (source and receiver) might lead to the creation of ground loops, with the result of current flowing through the shield. In this case, the shield acts like an antenna and the purpose of the shielding is lost.

The shielding concept also applies to grounding the chassis of the application if it is metallic. And it also helps remove EMI and EMC interference. In this case the mains earth ground is used to shield the chassis. Similarly DC ground can be used for shielding in case of the earth ground not being available.

Figure 28. Shielding technique

 

3.2.12 PCB layout recommendations

Separating the analog and digital layouts


It is recommended to separate the analog and digital circuitry on the PCB (see [Figure 29](#)). This also avoids tracks crossing each other. The tracks carrying digital signals may introduce high-frequency noise in analog signals because of coupling.

The digital signals produce high-frequency noise because of fast switching.

Coupling of a capacitive nature is formed due to the metal connections (tracks) separated by the dielectric provided by the PCB base (glass, ceramic or plastic).

It is recommended to use different planes for analog and digital grounds. If there is a lot of analog circuitry then an analog ground plane is recommended. The analog ground must be placed below the analog circuitry.

Figure 29. Separating the analog and digital layouts

 


Separating the analog- and digital-circuit power supplies

It is desirable to have separate analog and digital power supplies in cases where there is a lot of analog and digital circuits external to the microcontroller (see [Figure 30](#)). Depending on the STM32x package, different analog and digital power supply and ground pins are available. The V_{DDA}/V_{REF+} and V_{DD} pins can be powered from separate power supplies.

If you use a switching-type power supply for the digital circuitry, you should use a separate linear supply for the analog circuit. Also, if you expect a lot of noise on the DC power supply due to I/O switching etc., it is preferable to use a separate supply for the analog circuit.

Figure 30. Separating the analog and digital supplies

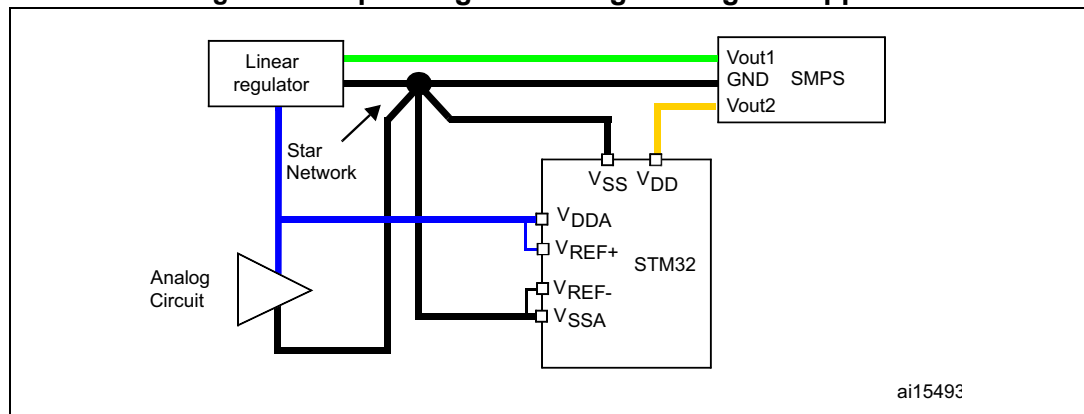

It is also recommended to connect the analog and digital grounds in a star network. This means that you must connect the analog and digital grounds at only one point. This prevents the introduction of noise in the analog power supply circuit due to digital signal switching. This also prevents current surges from affecting the analog circuit.

Using separate PCB layers for the supply and ground

- Two-layer PCBs

For two-layer PCBs, it is recommended to provide a maximum ground plane area. The power supply (V_{DD} , V_{DDA}) should run through thick tracks. The two layers can have their ground shorted together via multiple connections in the overlap region if the two layers feature the same ground signals. The unused PCB area can be used as the ground plane.

The other convention is to connect the unused PCB area on one layer to the positive supply (V_{DD}) and the unused area on the other layer, to ground. The advantage is a reduced inductance for power and ground signals. The maximum ground area provided for ground on the PCB results in a good shielding effect and reduces the electromagnetic induction susceptibility of the circuit.

- Multilayer PCBs

Wherever possible, try to use multilayer PCBs and use separate layers on the PCB for power and ground. The V_{DD} and V_{SS} pins of the various ICs can be directly connected to the power planes, thus reducing the length of track needed to connect the supply and ground. Long tracks have a high inductive effect. The analog ground can be connected at one point to this ground plane. If so, it should be close to the power supply.

A full ground plane provides good shielding and reduces the electromagnetic induction susceptibility of the circuit.

- Single-layer PCBs

Single-layer PCBs are used to save cost. They can be used only in simple applications when the number of connections is very limited. It is recommended to fill the unused area with ground. Jumpers can be used to connect different parts of the PCB.

3.2.13 Component placement and routing

Place the components and route the signal traces on the PCB so as to shield analog inputs.

Components like resistors and capacitors must be connected with very short leads. You can use surface-mounted device (SMD) resistors and capacitors. You can place SMD capacitors close to the microcontroller for decoupling purposes.

Use wide tracks for power, otherwise the series resistance of the tracks would cause a voltage drop. Indeed, narrow power tracks have a non-negligible finite resistance, so that high load currents through them would cause a voltage drop across them.

Quartz crystals must be surrounded by ground tracks/plane. The other side of the two-layer PCB below the crystal should preferably be covered by the ground plane. Most crystals have a metallic body that should be grounded. You should also place the crystal close to the microcontroller. You can use a surface-mounted crystal.

3.3 Software methods to improve precision

- Averaging samples:
 - averaging decreases speed but can give improved accuracy
- Digital filtering (50/60 Hz suppression from DC value)
 - set proper sampling frequency (the trigger from timer is useful in this case)
 - perform software post-processing on sampled data (e.g.: comb filter - for 50 Hz noise and its harmonics suppression)
- Fast Fourier Transform (FFT) for AC measurements:
 - to show harmonic parts in measured signal
 - slower, due to the use of more computation power
- Calibration of ADC: offset, gain, bit weight calibration
 - decreases internal ADC errors
 - internal ADC structure must be known
- Minimizing internal noise generated by CPU
 - design firmware to use minimum disturbance from microcontroller during ADC conversion - digital silence.

3.3.1 Averaging samples

The principle of this method is to increase ADC precision but decrease ADC conversion speed (oversampling). If the measured analog signal produces unstable ADC values, then the mean value of the given input signal can be obtained by averaging a set of values. Variation can be caused by signal noise or noise generated by the microcontroller itself (high speed digital signals capacitively coupled to the analog input signal).

Averaging is performed by choosing an appropriate number of samples to be averaged. This number depends on the required precision, minimum conversion speed and the level of other ADC errors (if another error has a greater influence on ADC precision, then increasing the number of averaging values has no effect on total measurement precision).

The advantage of this method is improving precision without any hardware changes. The disadvantage is lower conversion speed and therefore also lower frequency response (it is equivalent to decreasing effective sampling frequency).

3.3.2 Digital signal filtering

This method uses digital signal processing techniques.

In principle, averaging is also a simple digital filter with a specific frequency response. But if the noise frequency spectrum is known, a digital filter can be designed which minimizes noise influence and maximizes ADC frequency response. For example, if the noise in the measured signal is coming from the 50Hz power lines, then an appropriate digital filter suppresses only the 50 Hz frequency and delivers data signal without this noise.

The disadvantage of this method is that it needs appropriate microcontroller processing power and resources: CPU speed, data/program memory usage.

3.3.3 FFT for AC measurement

In some specific cases the application needs to know the amplitude of an AC signal with a given frequency. In this case the effective value of an AC signal can also be obtained by using a relatively slow sampling speed (in comparison to the measured signal frequency). For example, when measuring an AC mains signal (which is near-to-sinusoidal and has relatively low harmonics content), it is sufficient to choose a sampling frequency 32 times greater than the mains frequency (50 Hz). In this case you can obtain harmonics of up to the 15th order. The amplitude of 15th harmonics in the main signal is very small (the next order harmonics can be neglected). The calculated effective value of the mains signal is obtained with high precision because the effective values of harmonics are added to the total AC harmonic value as:

$$U_{\text{ef}} = \sqrt{U_1^2 + U_2^2 + \dots + U_n^2}$$

So if the 15th harmonics amplitude is only 1% (0.01) from the 1st harmonics (50 Hz) then its contribution to the total effective value will be only 0.01% (because of the above equation - square addition: $0.01^2 = 0.0001$).

The principle of this method is therefore to sample the AC signal with a known frequency and then perform post-processing on the FFT for each measured period. Because the number of sampling points per measured signal period is small (32 points for example) then the performance needed for FFT processing is not so high (only 32-point FFT for example).

Advantages: this method is good for AC measurement of signals with lower distortion.

The disadvantage is the requirement for precise signal sampling:

- The frequency of the measured signal must be known and the ADC sampling frequency must be set exactly as a 2^n multiplier of the measured frequency.
- The input signal frequency is measured by another method.
- The ADC sampling frequency is tuned by programming the prescaler and MCU master clock selection (if sampling is performed with an inaccurate clock an interpolation can be used to obtain samples at the required points).

3.3.4 ADC calibration

This method requires knowledge of internal ADC structure and how the ADC converter is implemented inside the microcontroller. This knowledge is necessary in order to design a physical/mathematical model of the ADC implementation.

A proper physical model (which is usually a schematic diagram) is used as the base for describing it mathematically. From the mathematical model, each element in the model can be obtained by a set of equations (for example, resistor/capacitor values which represent bit weights). To solve these equations, it is necessary to perform a set of practical measurements and obtain a set of solvable equations.

From the measured values and mathematical computation of the model, all known values of model elements (resistors, voltages, capacitors,...) can be put into the schematic diagram.

So instead of the ADC schematic with the designed values, you obtain an ADC schematic with the real values for a given microcontroller.

Computed model parameters are stored in the microcontroller memory after calibration and used in post-processing to correct ADC values.

3.3.5 Minimizing internal CPU noise

When the CPU operates, it generates a lot of internal and external signal changes which are transferred into the ADC peripheral through capacitive coupling. This disturbance influences ADC precision (unpredictable noise due to different microcontroller operations).

To minimize influences of the CPU (and of other peripherals) on ADC, it is necessary to minimize digital signal changes during sampling and conversion time (digital silence). This is done using one of the following methods (applied during sampling and conversion time):

- minimizing I/O pin changes
- minimizing internal CPU changes (CPU stop, wait mode)
- stopping clock for unnecessary peripherals (timers, communications...)

3.4 High impedance source measurement

This section describes the ADC measurement behavior of STM32x ADC when a signal source with high internal impedance is used. It explains how to design an application to reach the requested precision and provides workarounds.

3.4.1 ADC input stage problem

The ADC in STM32x devices is a switched-capacitor ADC type. Switched capacitors work also as sampling capacitors (see [Section 1.1](#) for a detailed explanation).

When a signal comes from a voltage source with high internal impedance (for instance, 150 kΩ), an added error can be seen in measurement results. Error signals have also been observed on the ADC input pin, as shown in [Figure 33](#) (if the voltage source has zero voltage: $U_{in} = 0\text{ V}$, $R_{in} = 150\text{ k}\Omega$, $C_{ext} = 0\text{ pF}$):

Figure 31. Typical voltage source connection to ADC input


 


Figure 32. Noise observed on ADC input pin during ADC conversions

 


3.4.2 Explanation of the behavior

The explanation of this added pin noise and added measurement error (in case a signal source with high internal impedance is used) comes from the internal ADC structure: its input sampling circuit.


Figure 33 shows a simplified schematic of the input stage (sample and hold circuit).

Figure 33. ADC simplified schematic of input stage - sample and hold circuit

 

The spikes (noise) present on ADC input pin during conversions are related to the sampling switch (S1). If the switch is closed, some charge (coming from the sample and hold capacitor C_{sh} or caused by another effect) is transferred to the input pin. Then this charge starts discharging through the source impedance (R_{in}). The discharge process ends at the end of the sampling time (t_s) when the switch S1 is opened. The remaining undischarged voltage remains on the capacitor C_{sh} and ADC measures this voltage. If the sampling time (t_s) is too short, the remaining voltage does not drop under 0.5 lsb and ADC measurement shows an added error. Figure 34 shows this process.

Figure 34. ADC input pin noise spikes from internal charge during sampling process

 

Note that a non-zero external capacitance C_{ext} (parasitic pin capacitance) also exists, so during conversion time the pin capacitance is discharged through source impedance R_{in} .

3.4.3 Minimizing added errors


Workaround for high impedance sources

To solve the added error problem, you can increase the sampling time (T_S) configuring ADC settings in MCU firmware, so that you discharge the C_{sh} charge through the source impedance R_{in} . The time constant ($R_{in} \cdot C_{sh}$) is the reference for choosing the sampling time. To choose the sampling time cycles, use this formula (for max. error of 1/2 lsb, see also [Section 3.2.6](#)):

$$T_S \geq f_{ADC} \cdot (R_{in} \cdot C_{sh}) \cdot \ln(2^{N+1}) \quad [\text{cycles}]$$

The clock for ADC (f_{ADC}) is another important factor; slowing down the ADC clock increases the sampling time.

Figure 35. Effect of sampling time extension

 

If the maximum register value of the sampling time (T_S) setting is reached and the problem is still present, you need a more complex solution which is applicable also for measurements of source with extra high internal impedance (see the section [Workaround for extra high impedance sources](#) below).

Note that for this application you must take into account not only the internal sampling capacitance, but also any external parasitic capacitance (in parallel to C_{ext}), such as: pin capacitance, PCB path capacitance, etc.

Do not add any external capacitor (C_{ext}) to the input pin when applying this above workaround. Its capacity will increase the timing constant ($R_{in} \cdot C_{sh} \parallel C_{ext}$) and the problem will remain.

Workaround for extra high impedance sources

This workaround consists of 2 parts: a hardware change and a software change.

Hardware change:

The hardware change consists of adding a large external capacitor (C_{ext}) to the input pin. The capacity size connected to the input pin must reach the value that causes the discharging of the internal sampling capacity C_{sh} to the external capacitor C_{ext} without increasing the voltage on C_{ext} to more than 0.5 lsb.

Example:

If the internal capacitor ($C_{sh} = 16 \text{ pF}$) is charged to full scale (U_{max} , which corresponds to 4096 lsb), then the external capacitor C_{ext} must be charged at maximum 0.5 lsb voltage level (U_{lsb}) after discharging C_{sh} to it. The capacity of C_{ext} will then be:


$$C_{ext} \geq C_{sh} \cdot \frac{U_{max}}{U_{lsb}} = 16\text{pF} \cdot \frac{4096}{0.5} \approx 131\text{nF}$$

The closest larger standard value chosen here is: $C_{ext} = 150 \text{ nF}$.

If the internal sampling capacitor C_{sh} is not charged to full voltage range (4096 level) before sampling, you can calculate the C_{ext} value replacing "4096" in the formula above. Calculating with 4096 level gives precise measurement results also in the case of ADC input channels switching (C_{sh} was charged from different ADC input in the previous measurement).

A side effect of this hardware workaround is the cyclical charging of C_{ext} which must be taken into account. Each ADC conversion transfers charge from C_{sh} to C_{ext} . One transfer charges the C_{ext} below 0.5 lsb, as described above, but more transfers can charge C_{ext} to larger values if it is not discharged between two conversions. [Figure 36](#) shows an example of this scenario where the ADC measurement is performed faster.

Figure 36. Charging the external capacitor with too short time between conversions

 

Software change:

The side effect mentioned above can be solved by software. The objective is to create a delay in order to let C_{ext} discharge through R_{in} (not measure so often) giving enough "discharge time" between ADC conversions. The "discharge time" (t_C) is equal to the transferred charge from C_{sh} to C_{ext} (charging) and from C_{ext} to R_{in} (discharging). The assumption is that $C_{ext} \gg C_{sh}$.

$$Q_{charging} = Q_{sh} = C_{sh} \cdot U_{max}$$

$$Q_{discharging} = \frac{U_{lsb}}{R_{in}} \cdot \int_0^{t_C} e^{-\frac{t}{R_{in}C_{ext}}} dt$$

where:

U_{lsb} 0.5 lsb voltage level

U_{max} 4096 lsb voltage level (worst case)

$$Q_{charging} = Q_{discharging}$$

$$C_{sh} \cdot U_{max} = \frac{U_{lsb}}{R_{in}} \cdot \int_0^{t_C} e^{-\frac{t}{R_{in}C_{ext}}} dt$$

Simplification of the above formula gives the final formula for the required waiting time between conversions:

$$t_C = -(R_{in} \cdot C_{ext}) \cdot \ln \left[1 - \frac{C_{sh} U_{max}}{C_{ext} U_{lsb}} \right]$$

This final formula shows dependency between the external capacitor C_{ext} and the required waiting time between two conversions if the precision U_{lsb} is needed.

From the same formula you can see that the argument in logarithm must be positive and therefore there is a condition for the minimal value of C_{ext} :

$$\left[1 - \frac{C_{sh} U_{max}}{C_{ext} U_{lsb}} \right] > 0$$

$$1 > \frac{C_{sh} U_{max}}{C_{ext} U_{lsb}}$$

$$C_{ext} > C_{sh} \cdot \frac{U_{max}}{U_{lsb}}$$

Choosing a larger C_{ext} decreases more the time between conversions (t_C).

An extra large C_{ext} ($C_{ext} \gg C_{sh} \cdot \frac{U_{max}}{U_{lsb}}$) enables sampling more often.

However, increasing C_{ext} limits the frequency bandwidth of measurement signal (increasing the "external" timing constant $R_{in} \cdot C_{ext}$).

The formulas below show how to choose the optimal C_{ext} value: signal bandwidth in correlation with sample time. Signal bandwidth is characterized by an “external” timing constant, so optimal solution is to charge C_{ext} during t_C :

$$(R_{\text{in}} \cdot C_{\text{ext}}) = t_C$$

$$(R_{\text{in}} \cdot C_{\text{ext}}) = -(R_{\text{in}} \cdot C_{\text{ext}}) \cdot \ln \left[1 - \frac{C_{\text{sh}} U_{\text{max}}}{C_{\text{ext}} U_{\text{lsb}}} \right]$$

$$-1 = \ln \left[1 - \frac{C_{\text{sh}} U_{\text{max}}}{C_{\text{ext}} U_{\text{lsb}}} \right]$$

$$e^{-1} = 1 - \frac{C_{\text{sh}} U_{\text{max}}}{C_{\text{ext}} U_{\text{lsb}}}$$

After simplification we obtain the final formula for optimal C_{ext} :

$$C_{\text{ext}} = \frac{C_{\text{sh}} \frac{U_{\text{max}}}{U_{\text{lsb}}}}{1 - e^{-1}} \approx 1,58 \cdot C_{\text{sh}} \frac{U_{\text{max}}}{U_{\text{lsb}}}$$

and the corresponding waiting time between conversions:

$$t_C \approx -(R_{\text{in}} \cdot C_{\text{ext}}) \cdot \ln \left[1 - \frac{1}{1,58} \right] \approx (R_{\text{in}} \cdot C_{\text{ext}})$$

Practically the firmware must not program the ADC in continuous mode but only in single mode and must ensure that there will be a time gap between conversions with duration equal to t_C . This adding of waiting time is the software change which must be applied together with the hardware change (adding an external capacitor C_{ext}).

Without implementation of t_C waiting time in software (for instance, running a conversion just after the first one) the external capacitor C_{ext} will be cyclically charged from the C_{sh} capacitor. After a lot of cycles the voltage on C_{ext} will reach a quite high error value (as previously shown in [Figure 36](#)).

A practical example of implementation for STM32L1xx ADC is shown below:

$C_{\text{sh}} = 16 \text{ pF}$ ADC property
$R_{\text{in}} = 150 \text{ k}\Omega$ signal source property
$U_{\text{max}} = 4096 \text{ lsb}$ ADC property
$U_{\text{lsb}} = 0.5 \text{ lsb}$ required precision

$$C_{\text{ext}} = 1,58 \cdot C_{\text{sh}} \frac{U_{\text{max}}}{U_{\text{lsb}}} = 1,58 \cdot 16 \text{ pF} \cdot \frac{4096}{0.5} \approx 207 \text{ nF} \Rightarrow 220 \text{ nF}$$

$$t_C = -(R_{\text{in}} \cdot C_{\text{sh}}) \cdot \ln \left[1 - \frac{C_{\text{sh}} U_{\text{max}}}{C_{\text{ext}} U_{\text{lsb}}} \right] = -(150 \text{ k}\Omega \cdot 220 \text{ nF}) \cdot \ln \left[1 - \frac{16 \text{ pF} \cdot 4096}{220 \text{ nF} \cdot 0.5} \right] \approx 29891 \mu\text{s} \Rightarrow 30 \text{ ms}$$


3.4.4 Source of described problem - ADC design

The following sections list some possible causes for the charging of the internal sampling capacitor C_{sh} . This is not an exhaustive list; only the main possible sources of the ADC design are listed.

Parasitic switch capacitance effect

The sampling switch inside ADC sampling circuit (see [Figure 33](#)) is not ideal. In reality the sample and hold switch (S1) is designed as 2 transistors (PMOS and NMOS, see [Figure 37](#)):


Figure 37. Implementation of sampling switch

 

The switch is controlled by the gate voltages of transistors (inverted signal on PMOS transistor). This design is a standard bidirectional switch (for rail to rail range of input U_{in} voltages). Both transistors have parasitic capacitances between gate and source.

If those capacitances are charged (close to the switch), then their charge can be transferred to the sampling capacitor (see [Figure 38](#)).

Figure 38. Parasitic capacitances of sampling switch

 


This charging and discharging currents (PMOS and NMOS asymmetric capacitances) can cause charge transfer to sampling capacitor C_{sh} .

Internal charging of sampling capacitor

It is possible that after the conversion process (successive approximation process in SAR type of ADC) the sample and hold capacitor C_{sh} is charged to some voltage. The reason can be:

- some leakage current to C_{sh} (parasitic current inside ADC structure, see [Figure 39](#))
- residual charge transfer from the switches when ADC structure is switched back to default state before next conversion
- other reasons (related to internal ADC parasitic structures)

Figure 39. Parasitic current example inside ADC structure

 

4 Conclusion

This application notes describes the main ADC errors and then methods and application design rules to minimize STM32x ADC errors and obtain the best ADC accuracy.

The choice of method depends on the application requirements and is always a compromise between speed, precision, enough computation power and design topology. The published methods lead to a precision improvement and are optimized for the design of an ADC converter using the SAR (successive approximation register) principle.

5 Revision history

Table 2. Document revision history

Date	Revision	Changes
14-Nov-2008	1	Initial release.
16-Sep-2013	2	Extended to STM32Fx Series and STM32L1 Series devices. Added Section 1.1: SAR ADC internal structure . Added Section 3.4: High impedance source measurement . Added Section 3.3: Software methods to improve precision . Text improvements and additions. Changed the Disclaimer on the final page.

Please Read Carefully:

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein.

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

ST PRODUCTS ARE NOT DESIGNED OR AUTHORIZED FOR USE IN: (A) SAFETY CRITICAL APPLICATIONS SUCH AS LIFE SUPPORTING, ACTIVE IMPLANTED DEVICES OR SYSTEMS WITH PRODUCT FUNCTIONAL SAFETY REQUIREMENTS; (B) AERONAUTIC APPLICATIONS; (C) AUTOMOTIVE APPLICATIONS OR ENVIRONMENTS, AND/OR (D) AEROSPACE APPLICATIONS OR ENVIRONMENTS. WHERE ST PRODUCTS ARE NOT DESIGNED FOR SUCH USE, THE PURCHASER SHALL USE PRODUCTS AT PURCHASER'S SOLE RISK, EVEN IF ST HAS BEEN INFORMED IN WRITING OF SUCH USAGE, UNLESS A PRODUCT IS EXPRESSLY DESIGNATED BY ST AS BEING INTENDED FOR "AUTOMOTIVE, AUTOMOTIVE SAFETY OR MEDICAL" INDUSTRY DOMAINS ACCORDING TO ST PRODUCT DESIGN SPECIFICATIONS. PRODUCTS FORMALLY ESCC, QML OR JAN QUALIFIED ARE DEEMED SUITABLE FOR USE IN AEROSPACE BY THE CORRESPONDING GOVERNMENTAL AGENCY.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.

The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2013 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

